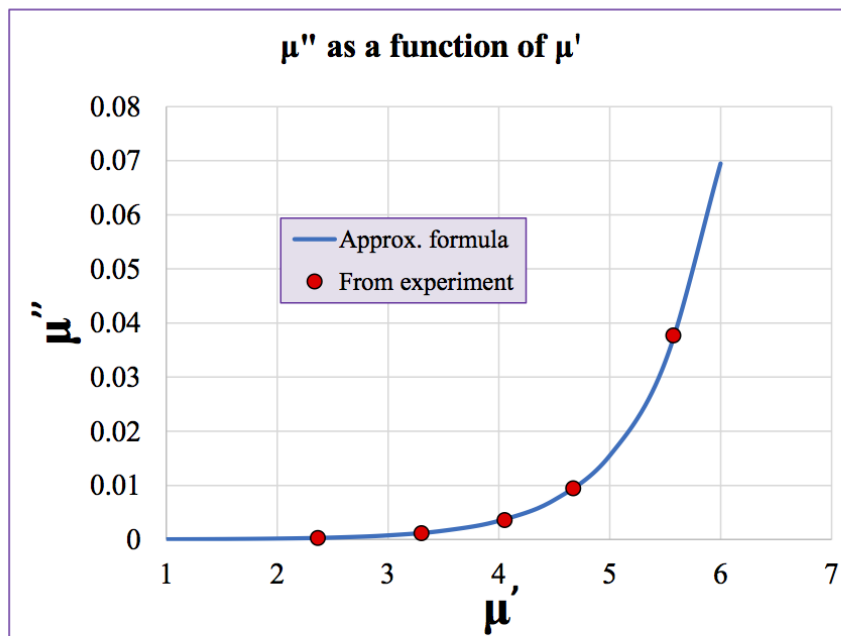


Summary of impedance, PA, and cathode resonator results with new AL800 μ measurements

C.Y. Tan
R. Madrak
02 Apr 2015

The new measurement

Function $\mu''=f(\mu')$ was derived from Robyn's measurements. It was assumed that $\tan\delta_E = 0.0001$, conductivity of copper $\sigma= 5.8 \cdot 10^7$ S/m, μ'' and μ' are averaged over garnet volume.




The experimental data is well approximated by formula:

$$\mu'' = 8.572 \cdot 10^{-6} \cdot e^{1.5\mu'}$$

μ'	μ''
1	3.8417E-05
1.5	8.1329E-05
2	0.00017217
2.5	0.00036449
3	0.00077163
3.5	0.00163353
4	0.00345819
4.5	0.00732099
5	0.01549854
5.5	0.03281041
6	0.06945964

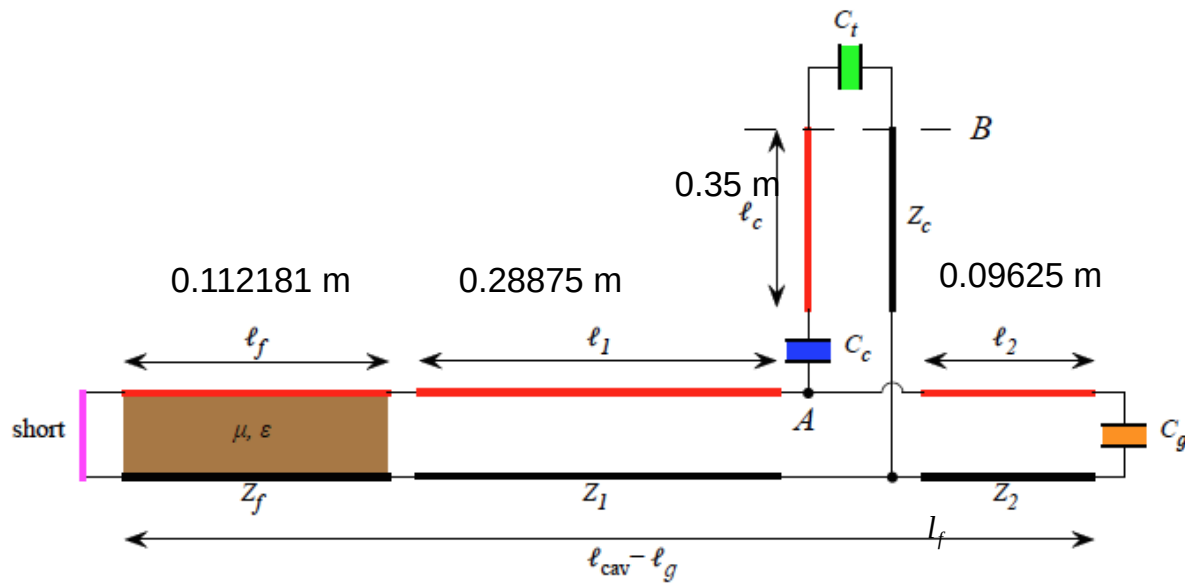
Summary of dimensions used in calculations




Parameter	value	comments
C_c	10 pF	Coupling capacitance
C_t	60 pF	Tube capacitance
C_g	3.4 pF	Gap capacitance
r_{fi}	0.105 m	Inner radius of ferrite
r_{fo}	0.170 m	Outer radius of ferrite

Parameter	value	comments
Z_1, Z_2	61.299 Ω	Non-ferrite characteristic impedance
Z_c	20.9269 Ω	Characteristic impedance of coupler

Equivalent circuit in ADS

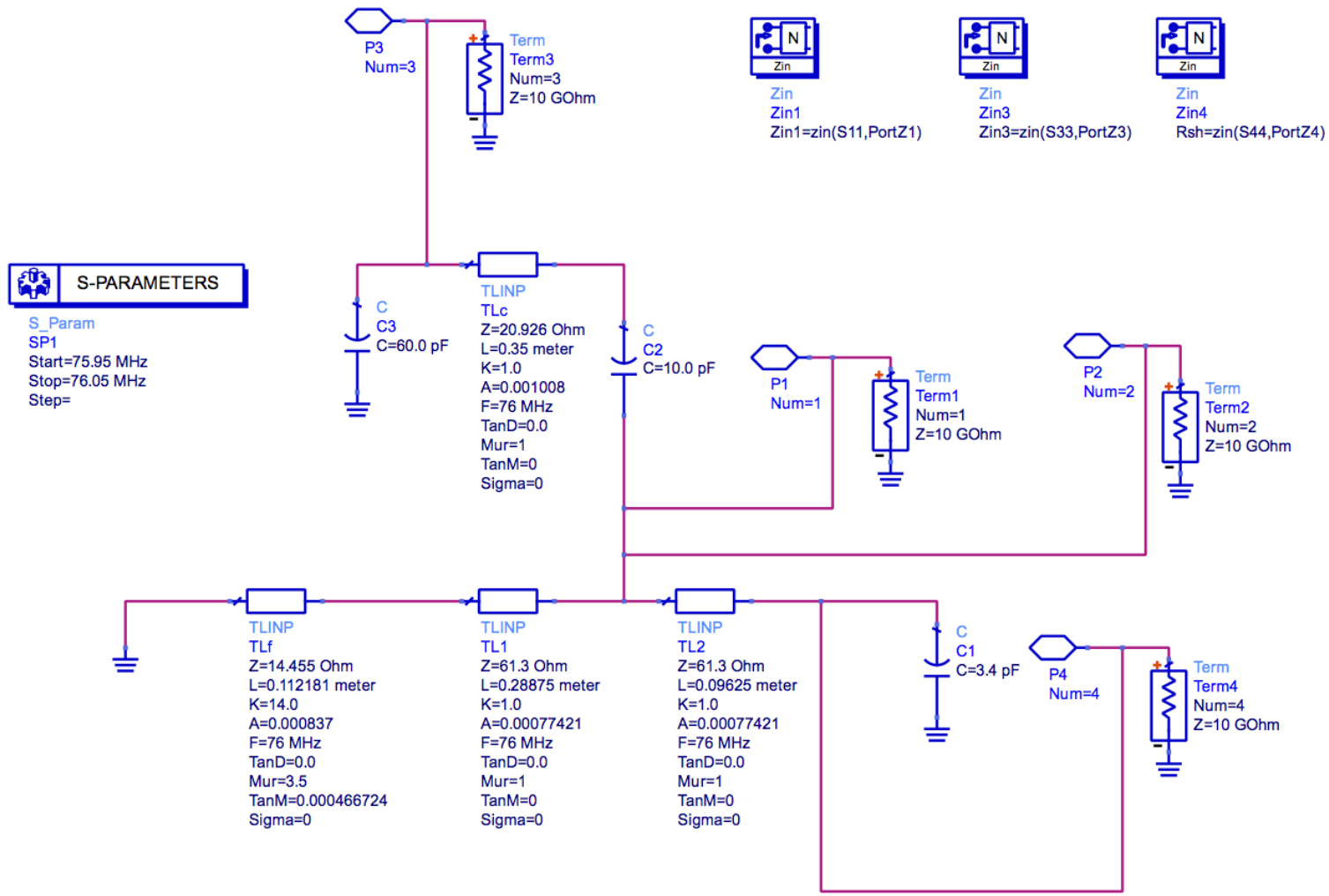




Example ADS results at 76 MHz

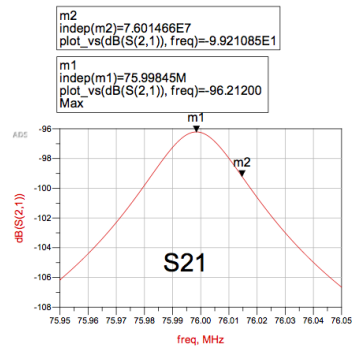



Q

...-indep(m3)))	...)-indep(m3))
<invalid>	2345.897

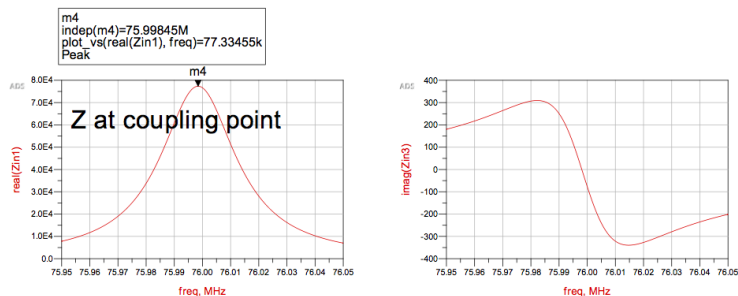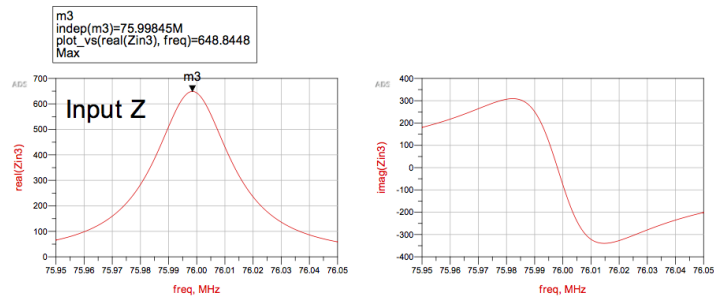
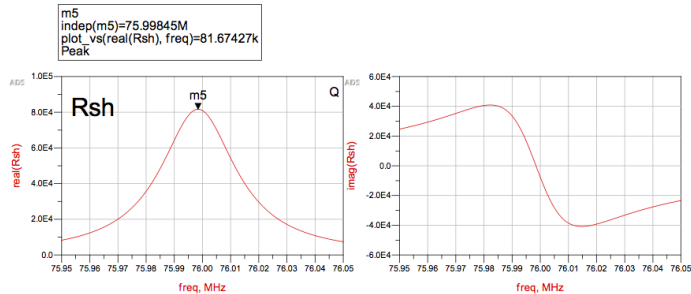
At 76 MHz:
Shunt impedance = 81.6 k Ω
 $R_{\text{anode}} = 649 \Omega$
Q = 2345



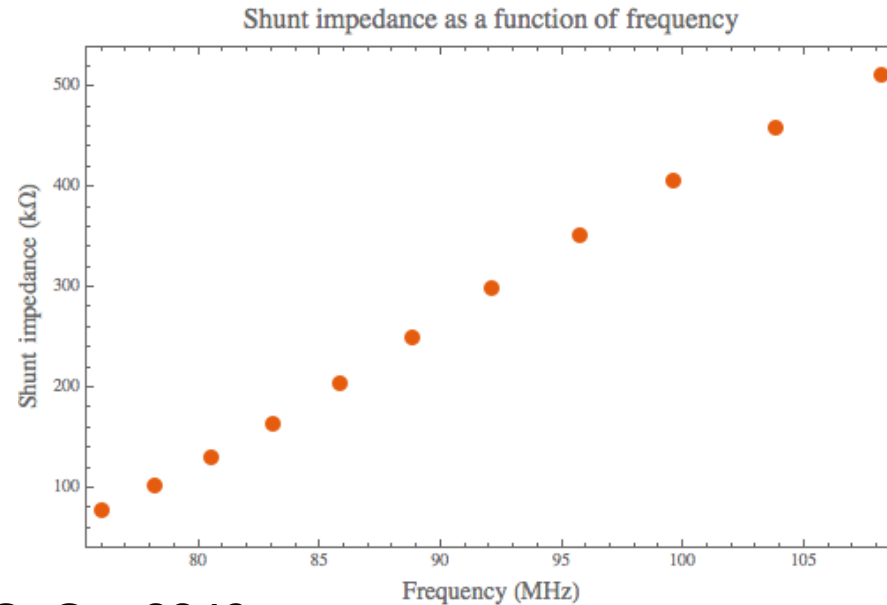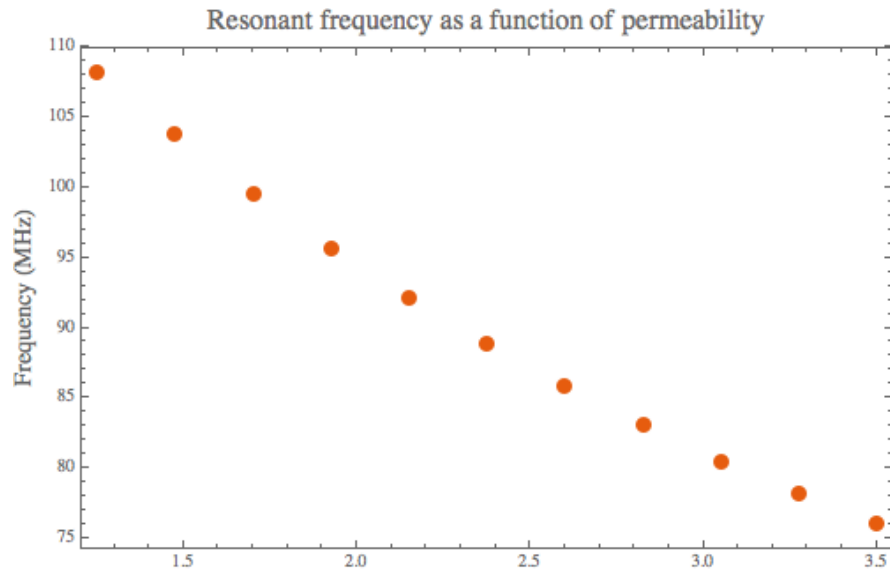
The following are results from Mathematica (essentially gives same results at 76 and 108 MHz with ADS)



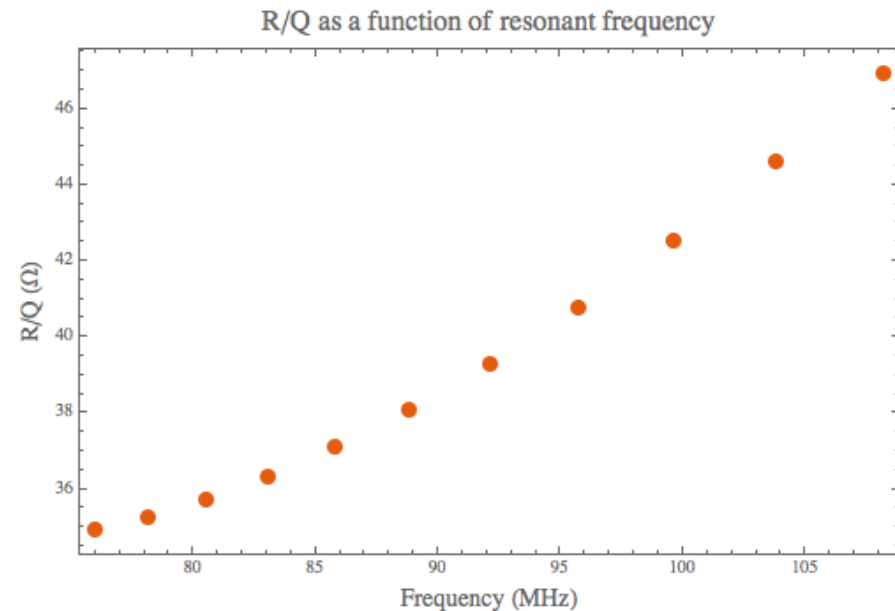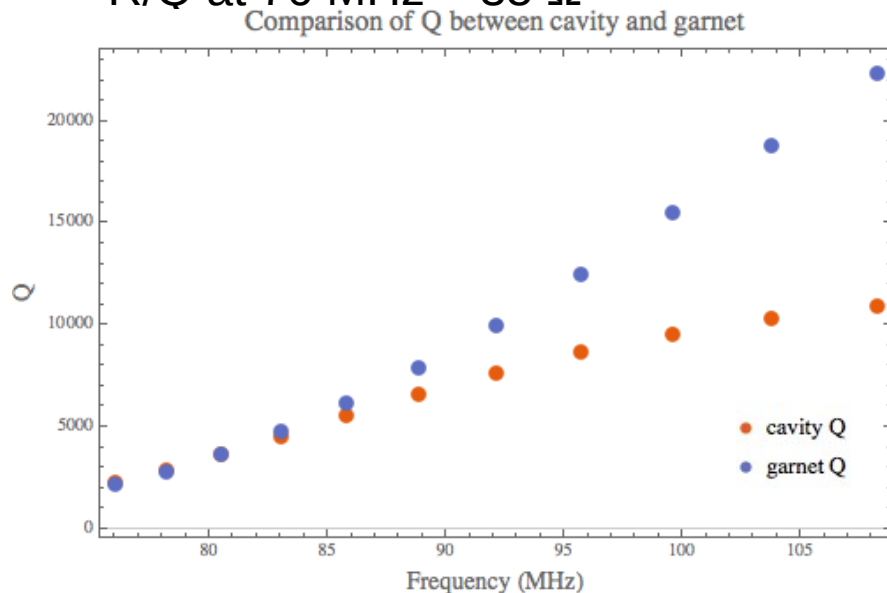
Shunt impedance at 76 MHz = 78.5 kΩ, $Q = 2249$
 R/Q at 76 MHz = 35 Ω




Anode impedance

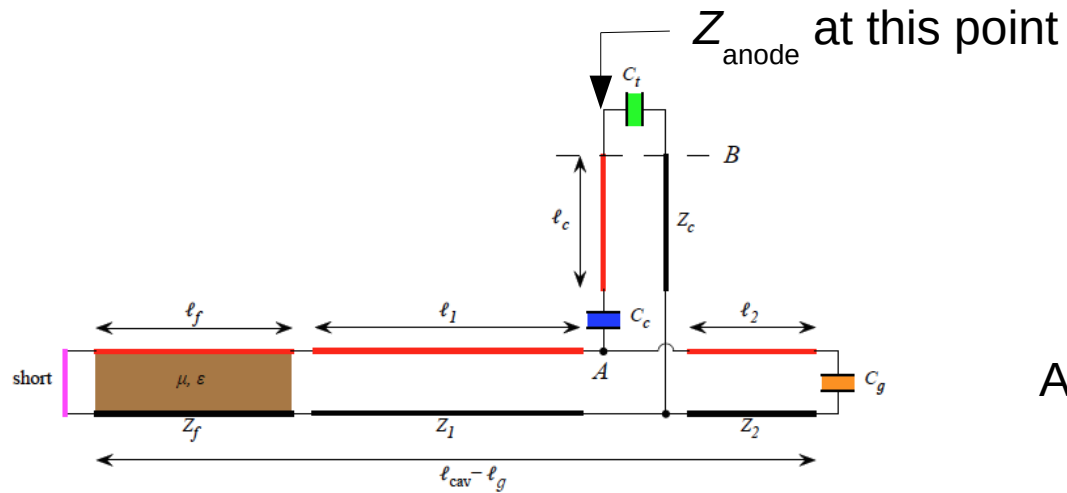

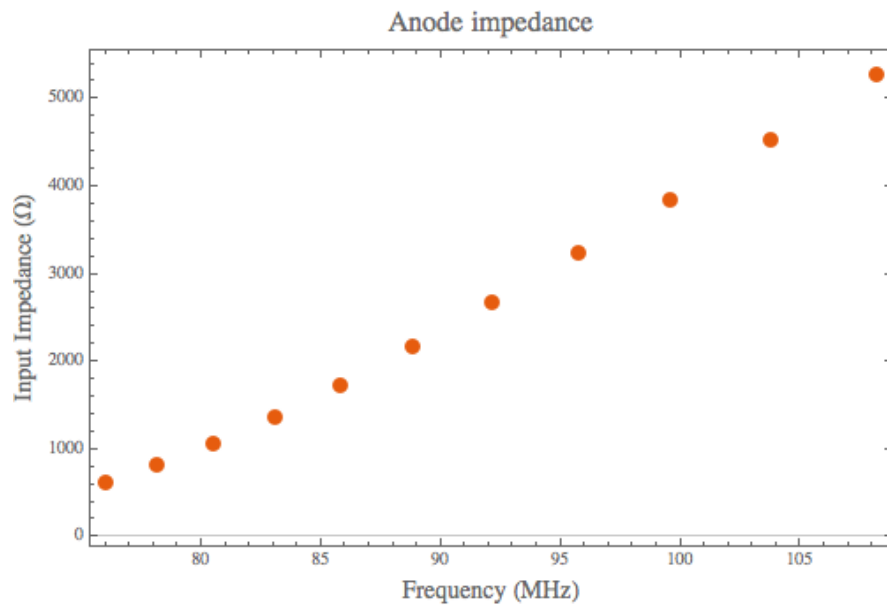
At 76 MHz = $R_{\text{anode}} = 624 \, \Omega$



Voltage along the cavity

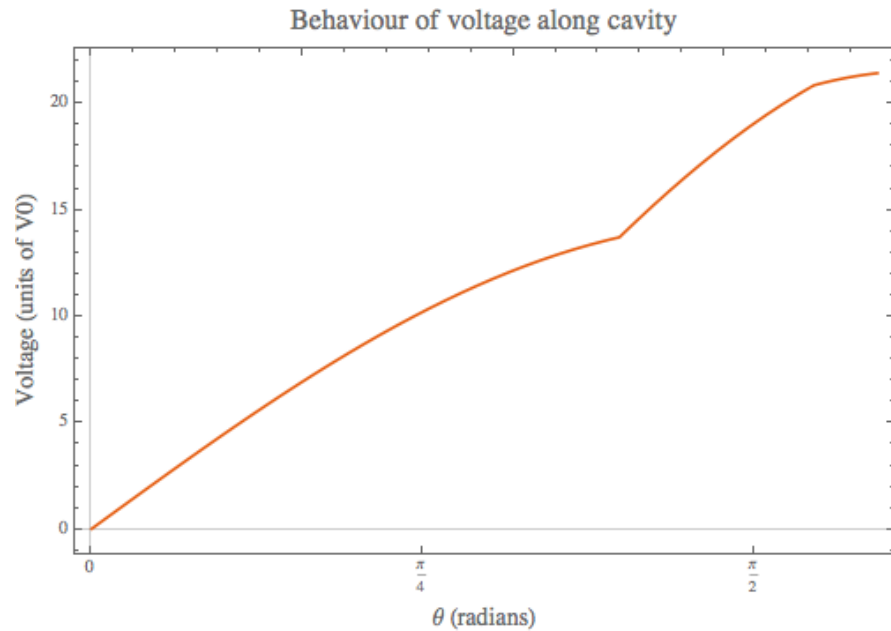


In terms of phase

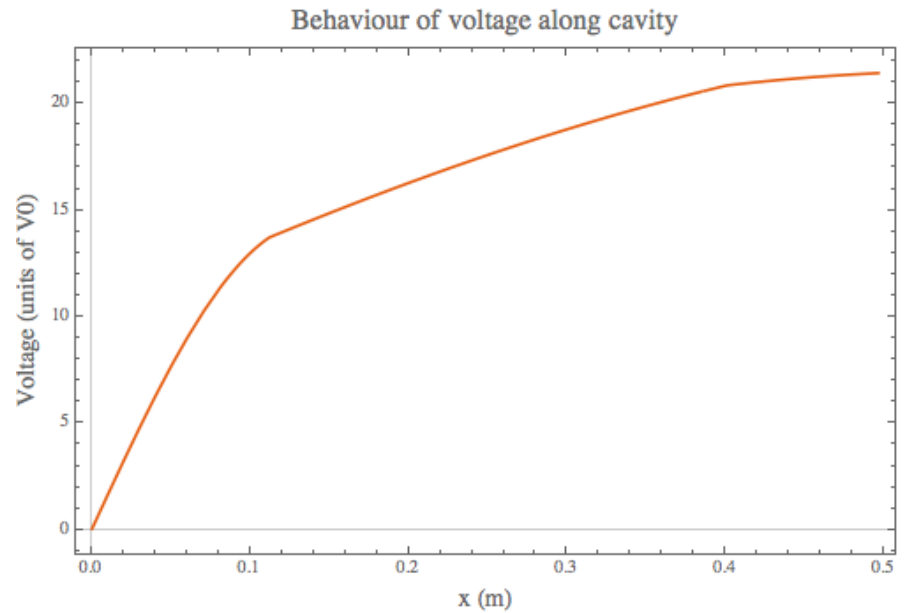

In terms of position


Stepup ratio

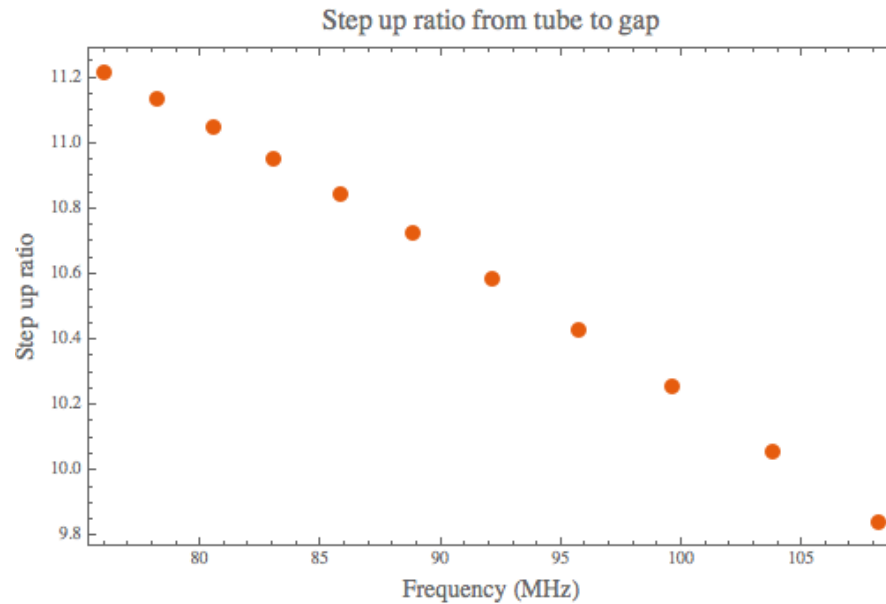

This is highly dependent on the coupling capacitance that we have chosen. Can be changed later.

Assume stepup is 10 for now.

Y567 Grounded Grid Load line

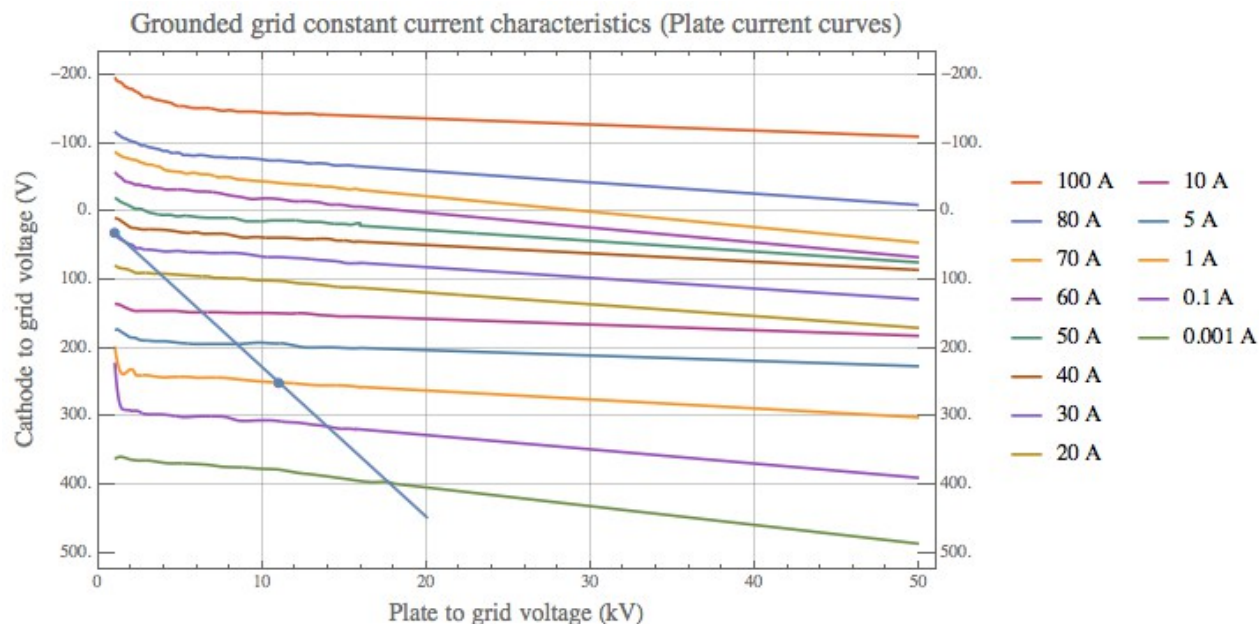


The two points that were chosen are:

Right hand point ($V_{anode} = 11 \text{ kV}$ – assuming stepup of 10, 1 kV screen voltage, and $V_{cathode} = 250 \text{ V}$ cathode to grid bias)

Left hand point ($V_{anode} = 1.025 \text{ kV}$ – screen to grid bias, $I_{peak} = 4 * I_0 = 31 \text{ A}$)

I_0 = takes into account the inefficiency of class B operation, $V_{gap} = 100 \text{ kV}$ and $R_{shunt} = 78.5 \text{ k}\Omega$.

Fourier components

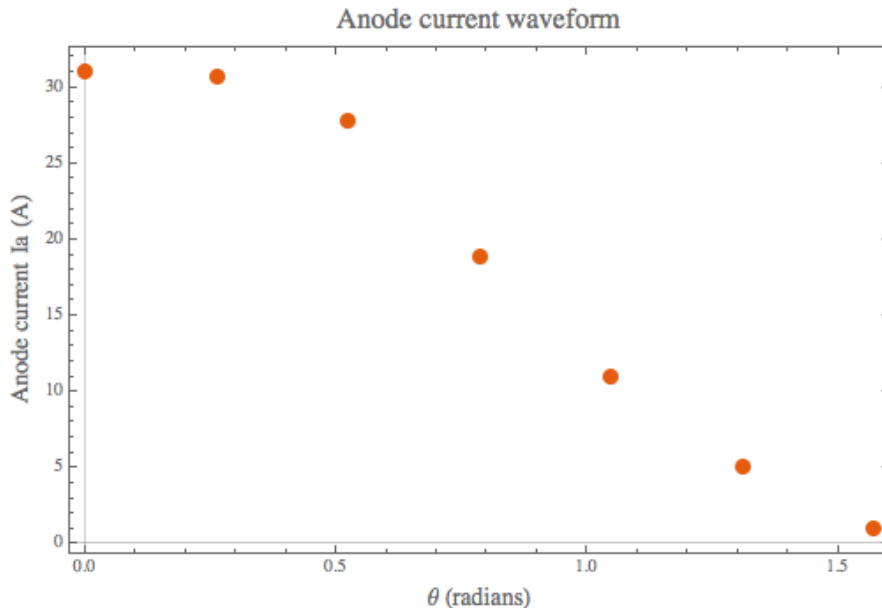

$I_{dc} = 8.8$ A, and thus DC input power $V_{anode} = 11$ kV $\Rightarrow P_{dc} = 96$ kW.


$I_{@76 \text{ MHz}} = 14.2$ A gives $P_{rf} = 71.3$ kW

Efficiency = 0.74

The load resistance (which I assume is the anode resistance) = 698Ω

This number is consistent with the anode resistance calculated earlier = 624Ω



Cathode side of the tube

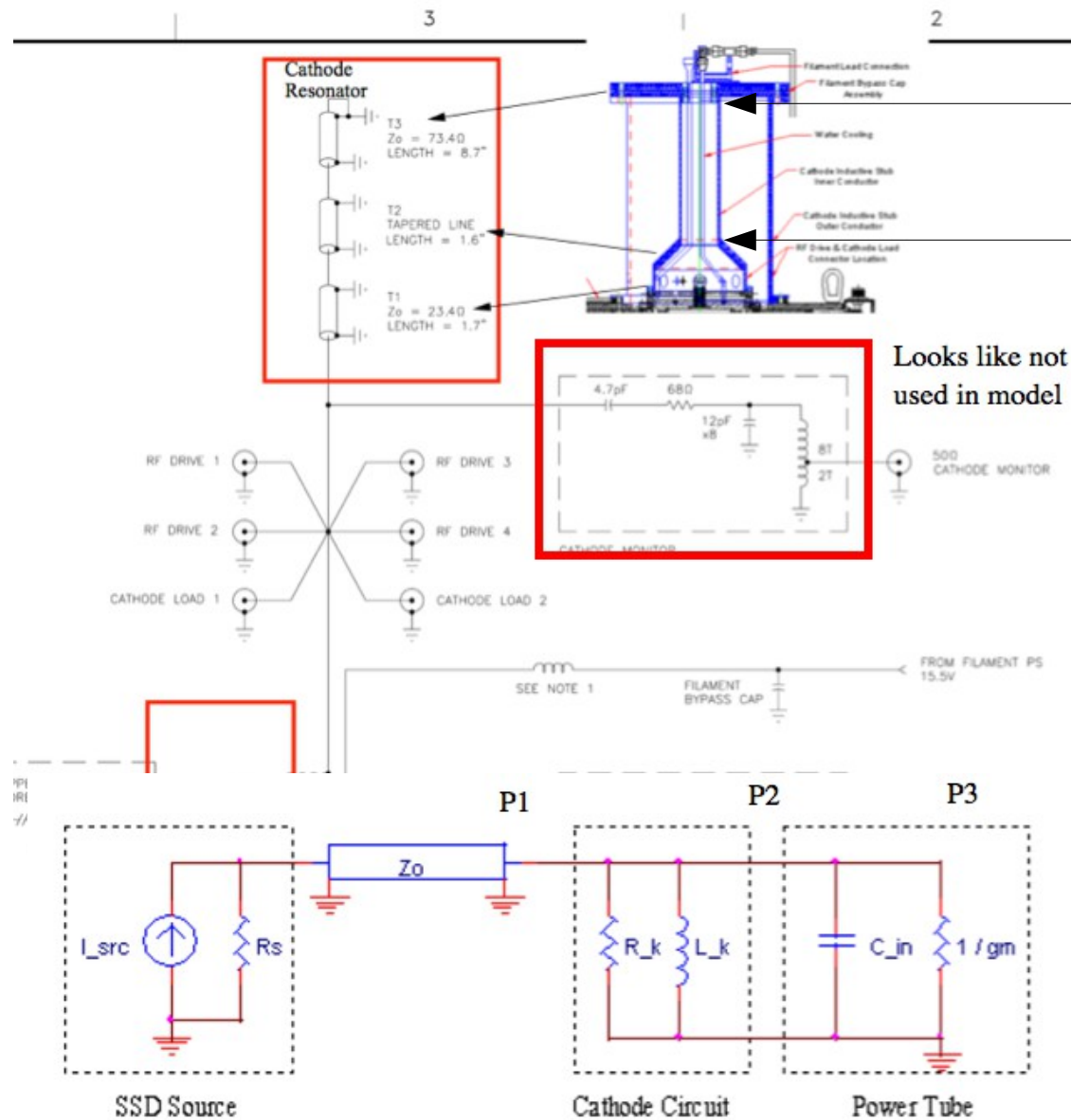

To get the cathode resonator to resonate between 76 MHz to 106 MHz, the length of this transmission line has been reduced from 22.1 cm to < 3.3 cm.

Looks like not used in model

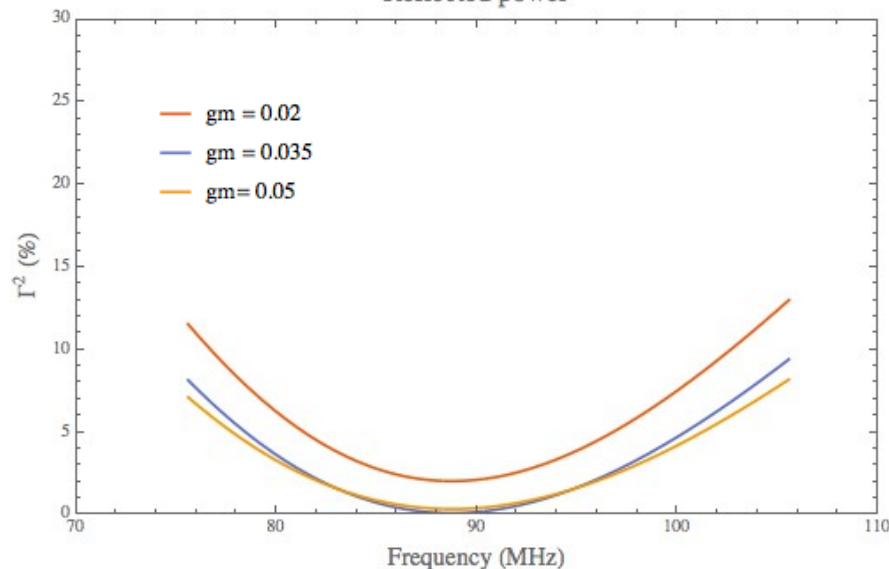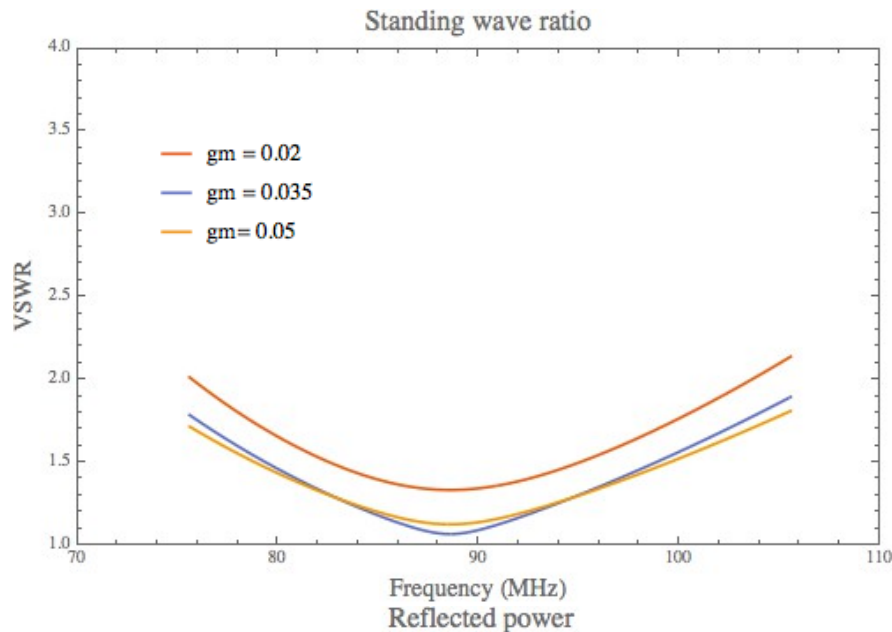Optimize to make VSWR more symmetric about frequency range




I reduced the length of L03 from 3.3 cm to 1.3 cm and reflections got a lot better across the frequency range. However, it is **worse** at 76 MHz. Although using gm=0.035, the power reflected is < 10%.


VSWR is now < 2 everywhere and reflected power < 12%.

Optimized results


Finding the resonance of the cathode

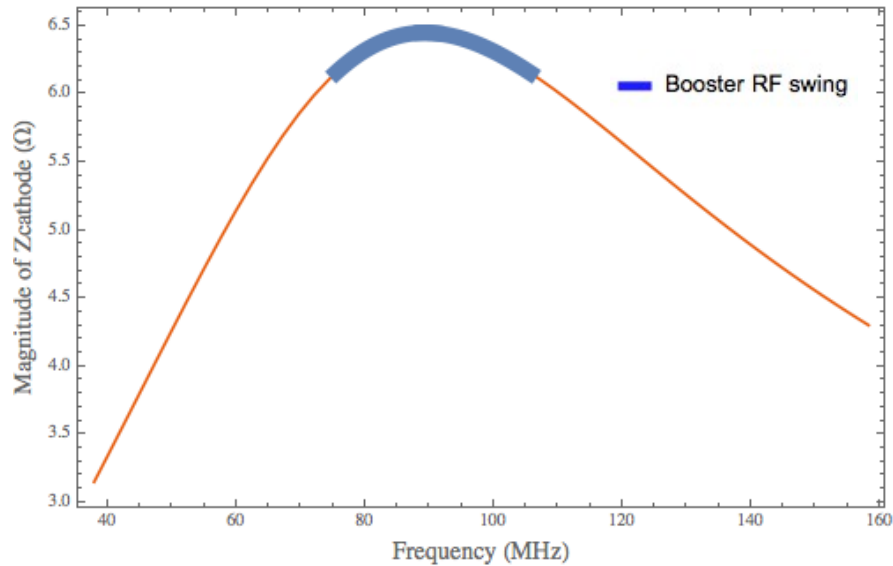


Voltage transfer function

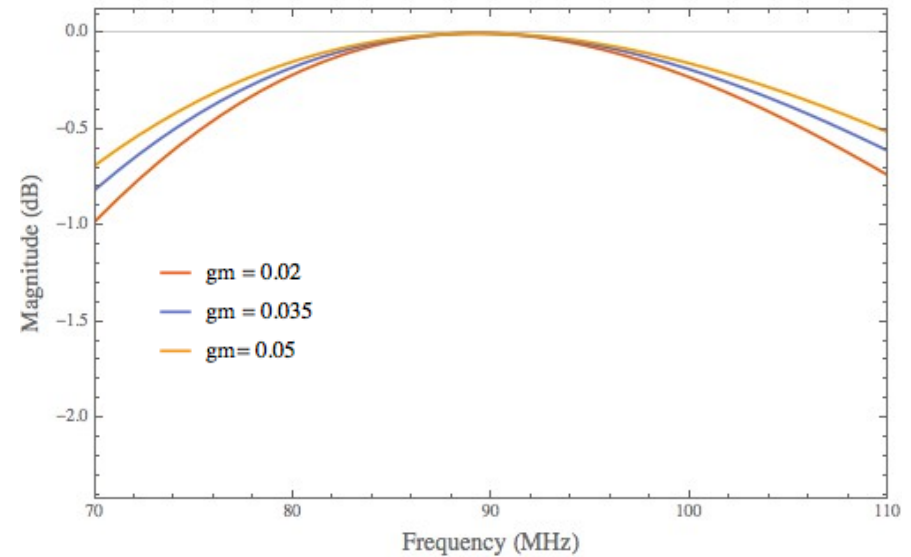



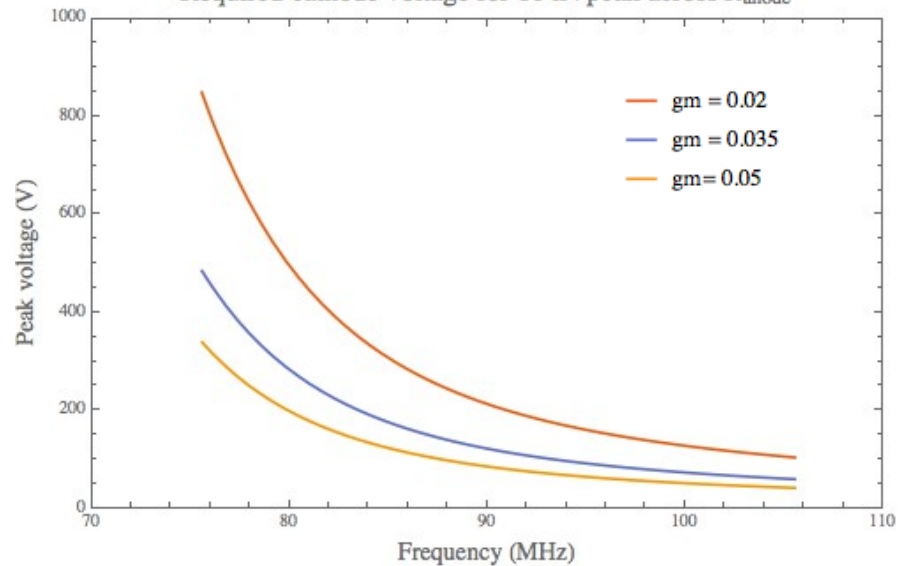
Required cathode voltage for 10 kVpeak across R_{anode}



Input impedance

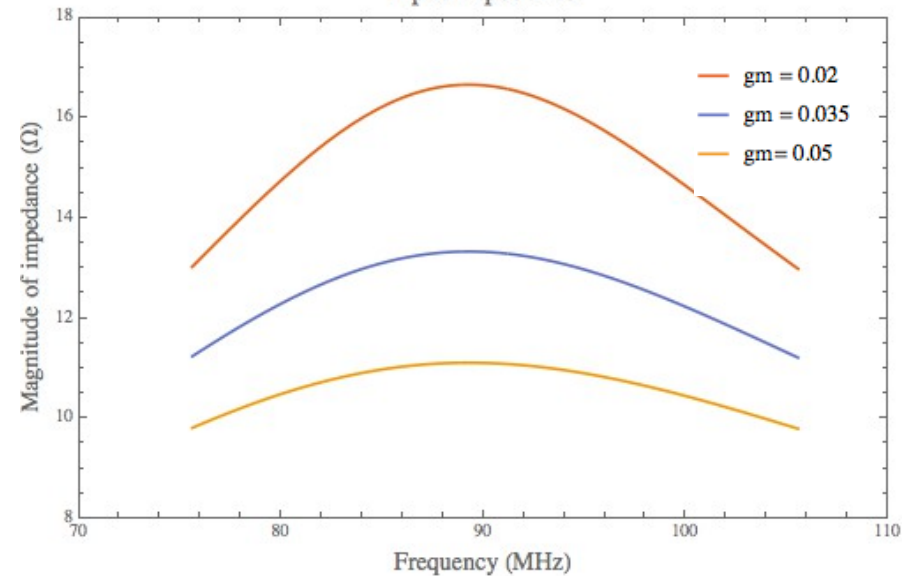

Optimized results (cont'd)

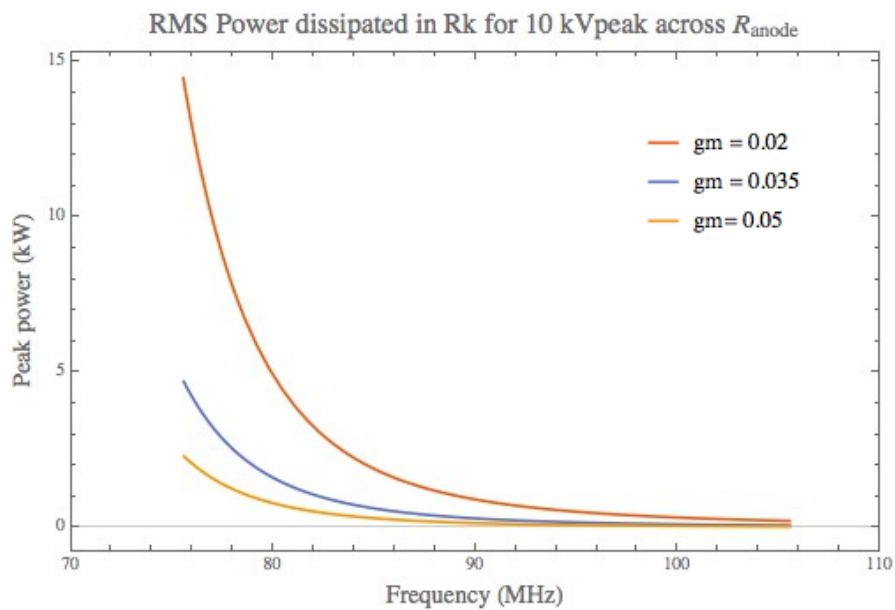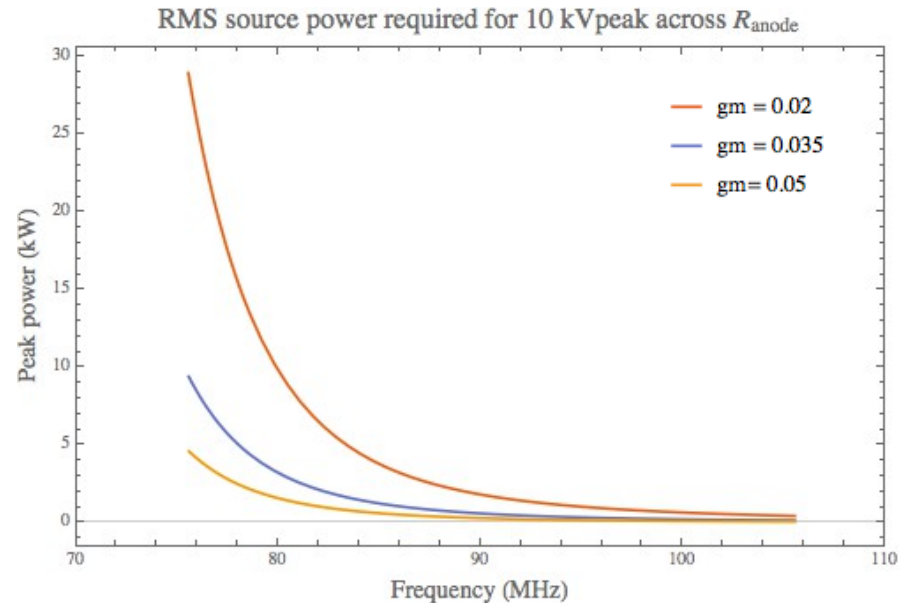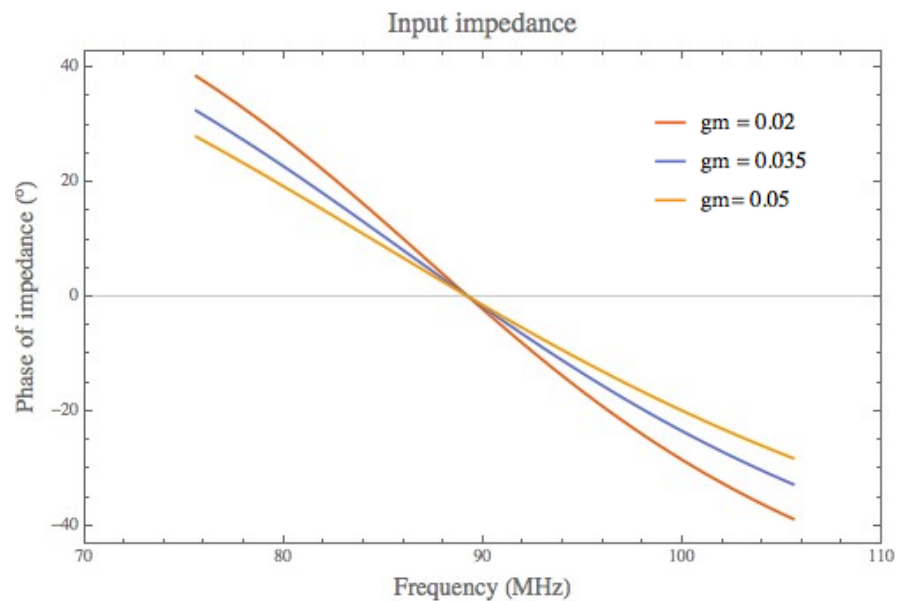

Summary

- No power reflection calculation because we had a wrong idea about the tube resistance being fixed at 1.4 k Ω .
 - Mismatch of PA to cavity comes from the tube not working completely in class B.
- Power requirements ~96 kW are reasonable for 100 kV gap voltage.
- Modifying cathode resonator does not seem to be too difficult.
 - Essentially one part of the present cathode resonator needs to be reduced in length to nearly zero length.
 - Need to build a test station with 76 – 106 MHz to show that the Y567 tube can supply the required power.